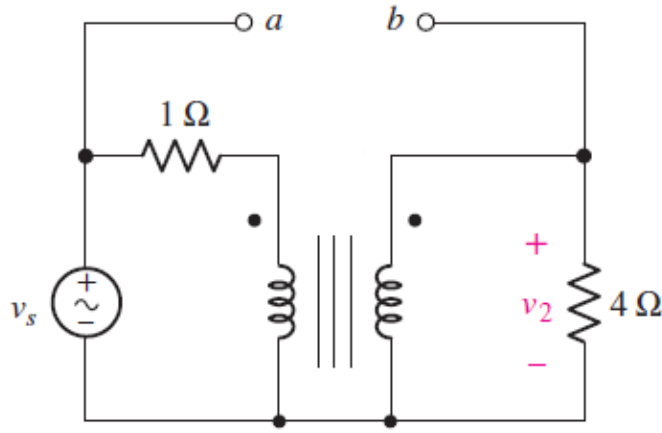


Set A:

Q1 [CO2] Consider $v_s = 117 \sin 500t \text{ V}$. The turn ratio is 30:1. Calculate v_2 if the terminals a and b are

(a) kept short-circuited.

(b) bridged by a 2Ω resistor.



Set B:

Q1 [CO2] Take turn ratio of 1:3 and $v_s = 720 \cos 120\pi t \text{ V}$, and calculate v_2 if terminals a and b are

(a) left open-circuited.

(b) bridged by a 10Ω resistor.